

Introduction to Electrical Engineering 2
Assignment Solution 1

Igor Shevtsov

September 5, 2014

1. Question 1 Solution

1.1 Section 1

Following equations describe current-voltage relations between some¹ circuit elements:

$$v_R = iR \quad (1.1)$$

$$i_C = C\dot{v}_C \quad (1.2)$$

$$v_L = L\dot{i}_L \quad (1.3)$$

Applying nodal method at the v_L node of circuit on Figure 1

$$I_0 = \frac{v_L}{R} + i_L \quad (1.4)$$

Using (1.3) one could obtain a differential equation

$$\dot{i}_L(t) + \frac{R}{L}i_L(t) = \frac{R}{L}I_0, t > 0 \quad (1.5)$$

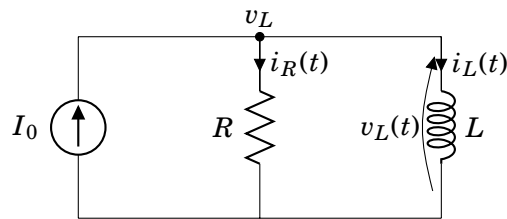


Figure 1: Electric Circuit

1.2 Section 2

Assuming circuit's steady state, yields constant² current, therefore

$$\text{ZSR: } i_L = I_0 \quad (1.6)$$

Proof. Solving ZIR of the equation (1.5) :

$$i_{L,ZIR}(t) = A \exp\left(\frac{-t}{\tau}\right) \quad (1.7)$$

$$\lim_{t \rightarrow \infty} i_L(t) = \lim_{t \rightarrow \infty} (i_{L,ZIR} + i_{L,ZSR}) = i_{L,ZSR} = I_0$$

□

¹Resistor, Capacitor and Inductor

²Resistor Shortened by Inductor

1.3 Section 3

Summarizing equation (1.6) with (1.7) and activating given initial condition $i_L(t = 0) = 2$ A results in final solution $i_L(t)$, where $\tau = \frac{L}{R}$:

$$i_L(t) = I_0 + (2 - I_0) \exp\left(\frac{-t}{\tau}\right), t > 0$$

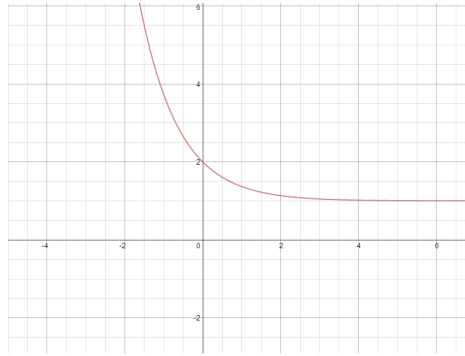


Figure 2: Inductor Current with $I_0 = 1$ A

2. Question 2 Solution

2.1 Section 1

Consider the circuit on Figure 3b. Now³ applying current divider technique one could easily calculate the following currents:

$$i_1 = \frac{40}{500 + 2k \parallel 6k} \cdot \frac{2k}{500 + 2k \parallel 6k}$$

$$i_2 = \frac{40}{500 + 2k \parallel 6k} \cdot \frac{6k}{500 + 2k \parallel 6k}$$

$$i_1(0^-) = 20 \text{ mA} \quad i_2(0^-) = 60 \text{ mA}$$

³Inductor is Short

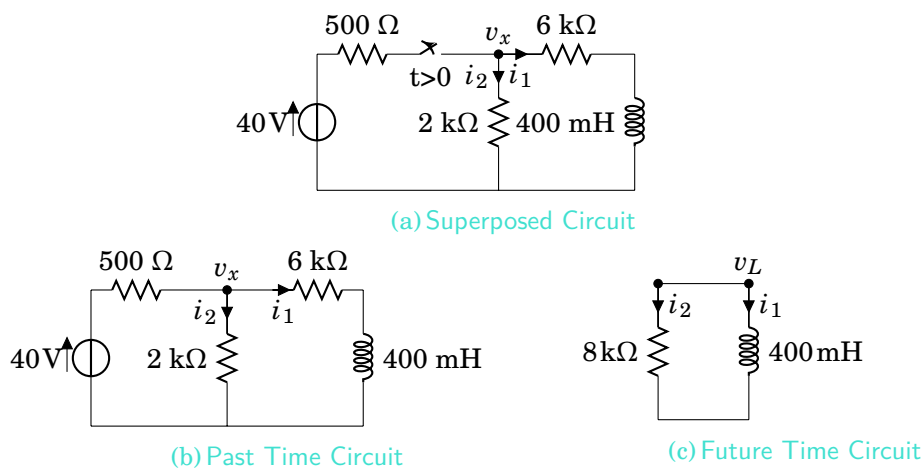


Figure 3: Question 2 Circuit

2.2 Section 2

Assuming continuity in the inductor current $i_1(0^-) = i_1(0^+) = 20\text{mA}$ on Figure 3c, where $i_1 = -i_2$, thus, setting $i_1(0^+) = -i_2(0^+) = 20\text{mA}$ we get the currents

$$i_1(0^+) = 20\text{mA} \quad i_2(0^+) = -20\text{mA}$$

2.3 Section 3

It's obvious, that circuits 3b and 3c are equivalent to the one on Figure 1 (Page 1) with $\tau = 50\text{ms}$ and $I_0 = V_0/R_{eq} = 20\text{mA}$:

$$\dot{i}_L(t) + \frac{R}{L}i_L(t) = \frac{R}{L}I_0 \quad , t > 0 \quad (2.8)$$

2.4 Section 4

Adopting ZIR⁴ solution (1.7)

$$i_1(t) = i_1(0^+) \exp\left(\frac{-t}{\tau}\right) \quad , t > 0$$

$$i_2(t) = -i_1(t)$$

⁴Since, there is no source in the circuit

3. Question 3 Solution

3.1 Section 1

The voltage drop on the capacitor⁵ on Figure 4b as follows

$$v_C(0^-) = 15 \text{ mA} \cdot 2.4 \text{ k}\Omega = 36 \text{ V} \quad (3.9)$$

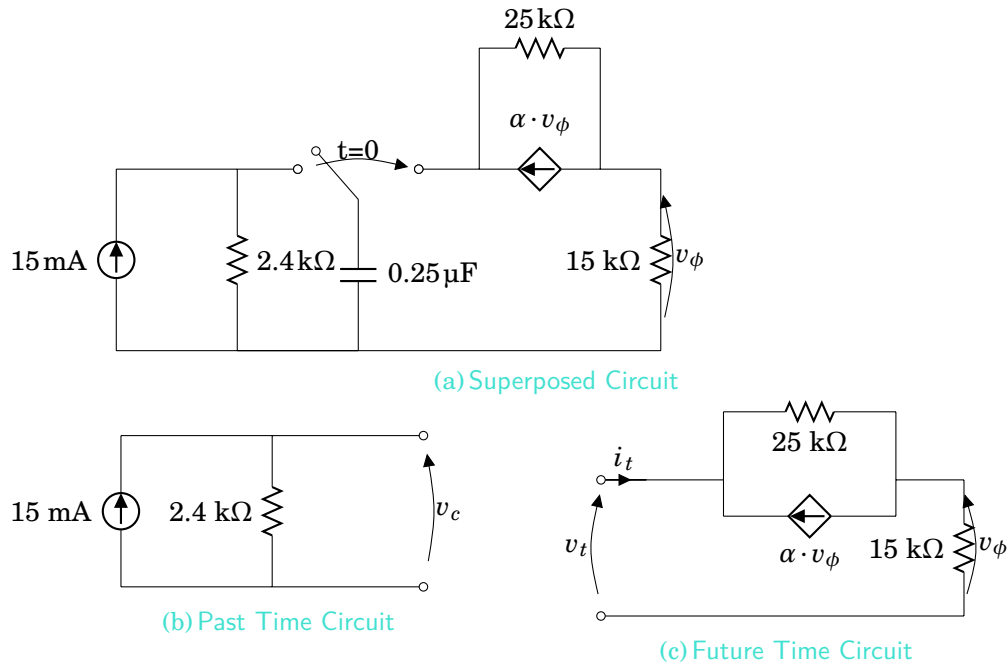


Figure 4: Question 3 Circuit

3.2 Section 2

Replacing capacitor with a test voltage, as shown on Figure 4c, allows input resistance calculation $R_{in} = \frac{v_t}{i_t}$

$$\begin{aligned} v_t - v_\phi &= 25k\alpha \cdot v_\phi \\ v_t &= (1 + 25k\alpha) \cdot v_\phi = 15k(1 + 25k\alpha) \cdot i_t \\ R_{in}(C) &= 15k(1 + 25k\alpha) \end{aligned} \quad (3.10)$$

⁵Open-Circuited Capacitor

3.3 Section 3

Given circuit's time constant $\tau = R \cdot C = 25$ ms requires resistor $R = 100$ k Ω . Setting into (3.10) leads to the value of α -parameter

$$\alpha \approx 2.26 \cdot 10^{-4}$$

3.4 Section 4

As before⁶ using ZIR solution (1.7) adapted for voltages, where $\tau = 25$ ms and initial condition of the capacitor⁷ $v_C(0^-) = v_C(0^+) = 36$ V

$$\left\{ \begin{array}{l} v_C(t) = v_C(0^+) \exp\left(\frac{-t}{\tau}\right) , t \geq 0 \\ v_C(t) = v_C(0^-) , t < 0 \end{array} \right.$$

⁶Due to circuits analogy

⁷Continuity in voltage drop